

## I Practice Problems: Circuit Analysis

### I.I Basics

**Problem 1:** Show the rules that govern how resistors and capacitors add:

---

*Part 1: Resistors*

---

(i) Series (*will be shown during the session*)

(ii) Parallel

---


*Part 2: Capacitors (use the technique that we discussed)*

---


(i) Series

(ii) Parallel

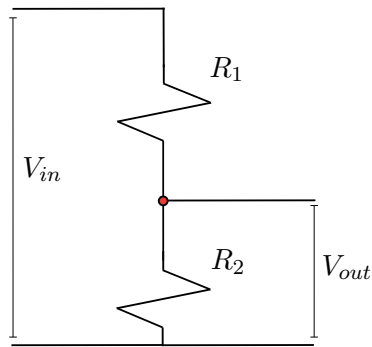**Problem 2:** We will be using our circuit analysis techniques to determine formulas for two commonly used topologies in circuit design: *voltage division* and *current division*.



(a) Voltage Divider.

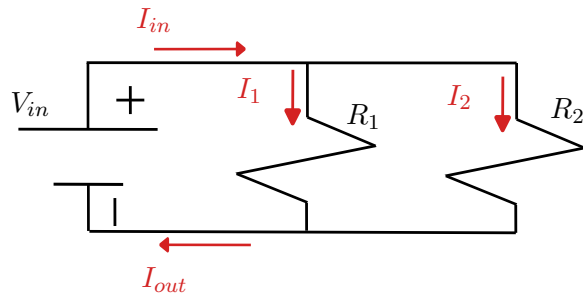

(b) Current Divider.

Figure 1: Common topologies.

(i) Determine  $V_{out}$  in Fig. 1a.

(ii) Determine  $I_1$  and  $I_2$  in Fig. 1b.

## I.II Node Voltage Method + Mesh Current Method

**Problem 3:** In Fig. 2 determine the voltages at  $V_x$  and  $V_y$  using node voltage method and state which of Kirchhoff's Laws you are employing.

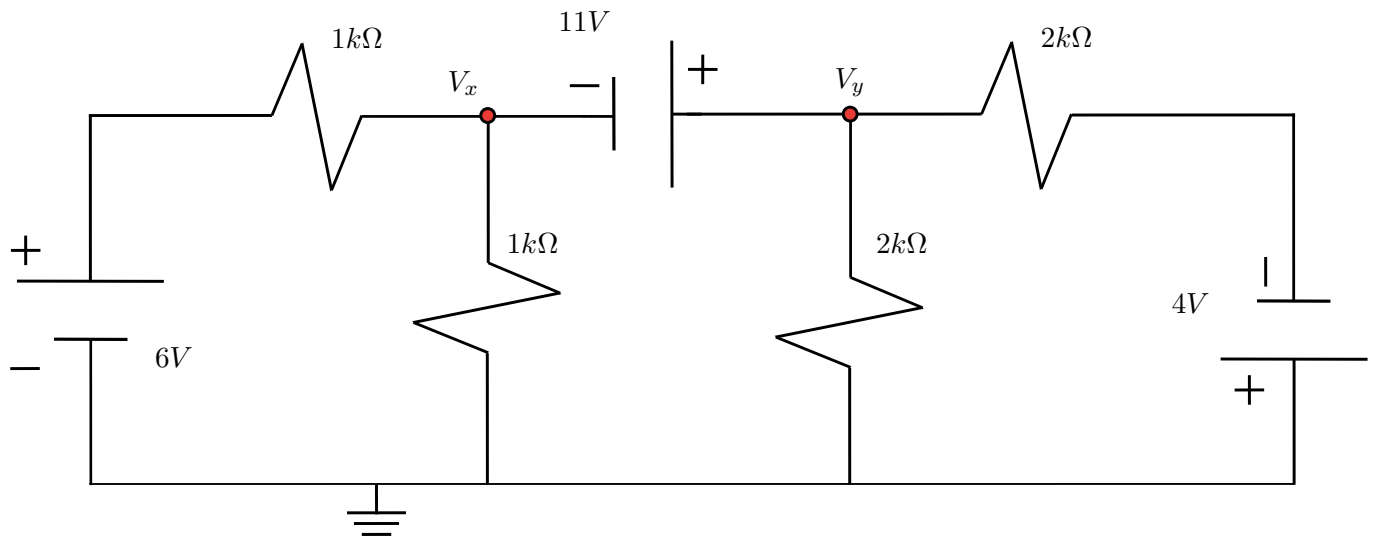


Figure 2: Simple Circuit.

**Problem 4:** Using mesh current method, determine the voltage at  $V_x$  in Fig. 3 and state which of Kirchhoff's Laws you are employing.

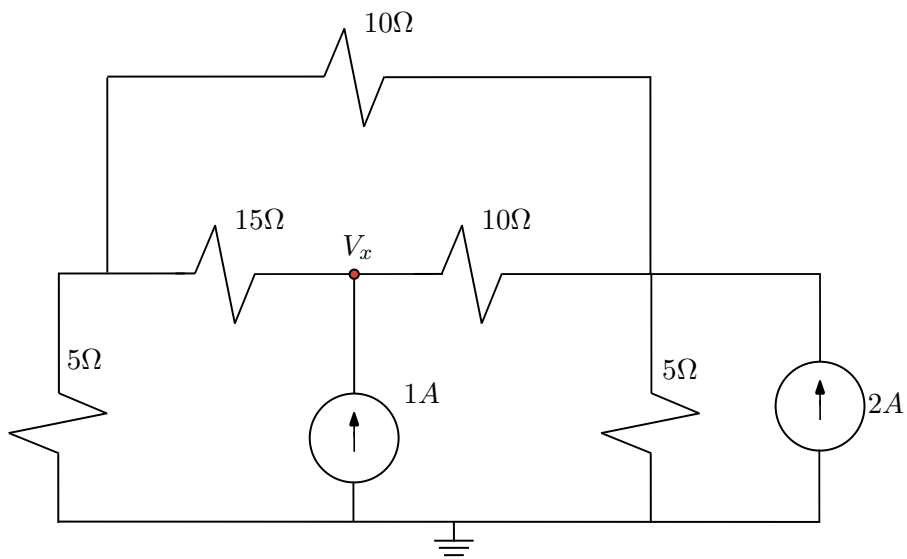


Figure 3: Simple Circuit.

### I.III Introduction to RC Circuits

**Problem 5:** All of the following questions refer to Fig. 4.

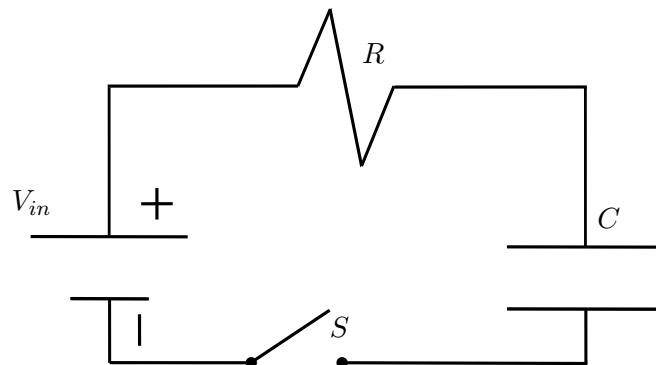


Figure 4: Simple RC Circuit.

- (i) If the switch  $S$  has been open for a long time, what is the voltage drop across the resistor?
  
- (ii) If we now close switch  $S$  and instantly look at the voltage drop across the resistor, what is it?
  
- (iii) If we now wait for a long time after closing the switch, what is the voltage across  $R$  and  $C$ . (*And what is the charge stored on the capacitor plates?*)

**Problem 5 (con't):**

(iv) Using differential equations, find an expression that describes the charge and current on the plates of the capacitor as a function of time.

**What are your major takeaways/things that you want to remember?**